



**Flinders
University**

Insert
Logo
Here

ENTER REPORT TITLE HERE

TEAM MEMBERS

Member One: XXXXX

Member Two: XXXXX

Member Three: XXXXX

Enter More....

2025-01-16

Contents

1 SECTION NAME	2
2 SECTION NAME	3
2.1 Sub Section Name	3
List of Tables	4
List of Figures	5
3 Raspberry Pi Hat Design	6
3.1 Design Requirements	6
3.2 Circuit Selection	6
3.3 Compoment Selection	6
4 Appendix A	9

1 SECTION NAME

*** ENTER TEXT HERE ***

2 SECTION NAME

*** ENTER TEXT HERE ***

2.1 Sub Section Name

*** ENTER TEXT HERE ***

List of Tables

List of Figures

3 Raspberry Pi Hat Design

After the previous season of Vex, it was realised that the existing solution for providing power to the Raspberry Pi was too bulky, which provided difficulty when packaging the robot. The previous solution existed of a battery pack that ran into a separate buck converter module, which lowered and regulated the voltage from the battery which then powered the Raspberry Pi. In order to make packaging the robot easier going into the next season, it was decided that the buck converter module could be incorporated into a hat, which directly interfaces with the Raspberry Pi.

3.1 Design Requirements

$$V_{in} \approx 12V \quad (1)$$

$$V_{out} = 5V \quad (2)$$

$$I_{out} = 6.5A \quad (3)$$

$$\Delta V < 150mV_{pk-pk} \quad (4)$$

$$Efficiency > 85\% \quad (5)$$

The Raspberry Pi has an operating voltage of $5V$, this is typically supplied over USB which has a nominal voltage ripple of $150mV_{pk-pk}$ therefore the buck converter must produce this voltage with any voltage ripple less than USB. As the buck converter will be operating from battery power, the input voltage will vary, however will be roughly $12V$. The Raspberry Pi also can draw a maximum current of $5A$ so it was decided that the converter will be able to be able to supply $6.5A$ in order to allow headroom for additional peripherals. Finally the efficiency of greater than 85% was selected in order to minimise the requirement for heatsinks or active cooling methods.

3.2 Circuit Selection

There are two types of buck converter circuits, synchronous and asynchronous, the asynchronous design is simpler to control as it only contains one MOSFET however at

3.3 Component Selection

In order to calculate the values of the components, the duty cycle, frequency and off time must be calculated.

$$d = \frac{V_{out}}{V_{in}} \quad (6)$$

$$d = \frac{5}{12} \quad (7)$$

$$d \approx 0.42 \quad (8)$$

For the frequency of the PWM signal used to drive the buck converter, $1mHz$ was selected as it provides a lower voltage ripple, lower under and overshoot voltages, and a smaller design footprint, as smaller capacitors and inductors are required.

$$f = 1mHz \quad (9)$$

$$f = 1 \times 10^6 Hz \quad (10)$$

$$\therefore T = 1 \times 10^{-6} s \quad (11)$$

$$t_{off} = T(1 - d) \quad (12)$$

$$t_{off} = 1 \times 10^{-6}(1 - 0.42) \quad (13)$$

$$\therefore t_{off} = 5.8 \times 10^{-7} s \quad (14)$$

Next is to calculate the value of the inductor, using the inductor equation $V = L \frac{di}{dt}$. The calculations will assume that the voltage Raspberry Pi.

$$V = L \frac{di}{dt} \quad (15)$$

$$\therefore L = \frac{\int V dt}{\Delta I} \quad (16)$$

$$L = \frac{V_{out} \cdot t_{off}}{\Delta I} \quad (17)$$

$$\Delta I = I_{min} \cdot 2 \quad (18)$$

$$\Delta I = 0.4 \cdot 2 \quad (19)$$

$$\Delta I = 0.8A \quad (20)$$

$$\therefore L = \frac{5 \cdot 5.8 \times 10^{-7}}{0.8} \quad (21)$$

$$\therefore L = 3.625 \times 10^{-6} H \quad (22)$$

$$L = 3.625 \mu H \quad (23)$$

Then the capacitor values can be calculated using the capacitor equation, $I = C \frac{dv}{dt}$. The current input will need to be calculated as a part of determining the capacitance required. Initially the discontinuous capacitance will be calculated, denoted by C_D , then the capacitance of the continuous capacitor will be calculated, denoted by C_C . The peak to peak voltage has also been decreased to account for the Equivalent Series Resistance (ESR) of the capacitors, which will greatly increase

the V_{pk-pk} .

$$P_{max} = 5V \cdot 6.5A \quad (24)$$

$$P_{max} = 32.5W \quad (25)$$

$$I_{in} = \frac{P_{max}}{V_{in}} \quad (26)$$

$$I_{in} = \frac{32.5}{12} \quad (27)$$

$$I_{in} \approx 3A \quad (28)$$

$$V_{pk-pk} = 0.01V \quad (29)$$

$$I = C \frac{dv}{dt} \quad (30)$$

$$\therefore C = \frac{\int I dt}{\Delta V} \quad (31)$$

$$\therefore C = \frac{I_{in} \cdot t_{off}}{\Delta V} \quad (32)$$

$$C_D = \frac{3 \cdot 5.8 \times 10^{-7}}{0.01} \quad (33)$$

$$C_D = 1.74 \times 10^{-4}F \quad (34)$$

$$C_D = 174\mu F \quad (35)$$

As the current across the continous capacitor is a triangular wave, the integral will be calculated using the area of a triangle, $A = \frac{1}{2}bh$.

$$C_C = \frac{\int I dt}{\Delta V} \quad (36)$$

$$\int I dt = \frac{1}{2}bh \quad (37)$$

$$b = \frac{T}{2} \quad (38)$$

$$h = \frac{\Delta I}{2} \quad (39)$$

$$\therefore \int I dt = \frac{\frac{T}{2} \cdot \frac{\Delta I}{2}}{2} \quad (40)$$

$$\int I dt = \frac{T \cdot \Delta I}{8} \quad (41)$$

$$\therefore C_C = \frac{T \cdot \Delta I}{8 \cdot \Delta V} \quad (42)$$

$$C_C = \frac{1 \times 10^{-6} \cdot 0.8}{8 \cdot 0.01} \quad (43)$$

$$C_C = 1 \times 10^{-5}F \quad (44)$$

$$C_C = 10\mu F \quad (45)$$

4 Appendix A